

# CURRENT ELECTRICITY

## 1. ELECTRIC CURRENT

$$I_{av} = \frac{\Delta q}{\Delta t} \text{ and instantaneous current}$$

$$i = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t} = \frac{dq}{dt}$$

## 2. ELECTRIC CURRENT IN A CONDUCTOR

$$I = nAeV_d$$

$$V_d = \frac{\lambda}{\tau}$$

$$V_d = \frac{\frac{1}{2} \left( \frac{eE}{m} \right) \tau^2}{\tau} = \frac{1}{2} \frac{eE}{m} \tau$$

$$I = neAV_d$$

## 3. CURRENT DENSITY

$$\vec{J} = \frac{dI}{ds} \vec{n}$$

## 4. ELECTRICAL RESISTANCE

$$I = neAV_d = neA \left( \frac{eE}{2m} \right) \tau = \left( \frac{ne^2 \tau}{2m} \right) AE$$

$$E = \frac{V}{\ell} \text{ so } I = \left( \frac{ne^2 \tau}{2m} \right) \left( \frac{A}{\ell} \right) V = \left( \frac{A}{\rho \ell} \right) V = V/R \Rightarrow V = IR$$

$\rho$  is called resistivity (it is also called specific resistance) and

$\rho = \frac{2m}{ne^2 \tau} = \frac{1}{\sigma}$ ,  $\sigma$  is called conductivity. Therefore current in conductors

is proportional to potential difference applied across its ends. This is **Ohm's Law**.

Units:

$R \rightarrow \text{ohm}(\Omega)$ ,  $\rho \rightarrow \text{ohm-meter}(\Omega\text{-m})$

also called siemens,  $\sigma \rightarrow \Omega^{-1}\text{m}^{-1}$ .

## Dependence of Resistance on Temperature :

$$R = R_0 (1 + \alpha \theta).$$

## Electric current in resistance

$$I = \frac{V_2 - V_1}{R}$$

## 5. ELECTRICAL POWER

$$P = V I$$

$$\text{Energy} = \int p dt$$

$$P = I^2 R = VI = \frac{V^2}{R}$$

$$H = VIt = I^2 R t = \frac{V^2}{R} t$$

$$H = I^2 R T \text{ Joule} = \frac{I^2 R T}{4.2} \text{ Calorie}$$

## 9. KIRCHHOFF'S LAWS

### 9.1 Kirchhoff's Current Law (Junction law)

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

### 9.2 Kirchhoff's Voltage Law (Loop law)

$$\sum IR + \sum \text{EMF} = 0.$$

## 10. COMBINATION OF RESISTANCES :

### Resistances in Series:

$R = R_1 + R_2 + R_3 + \dots + R_n$  (this means  $R_{\text{eq}}$  is greater than any resistor) and

$$V = V_1 + V_2 + V_3 + \dots + V_n$$


$$V_1 = \frac{R_1}{R_1 + R_2 + \dots + R_n} V; V_2 = \frac{R_2}{R_1 + R_2 + \dots + R_n} V;$$

### 2. Resistances in Parallel :

$$\boxed{\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$


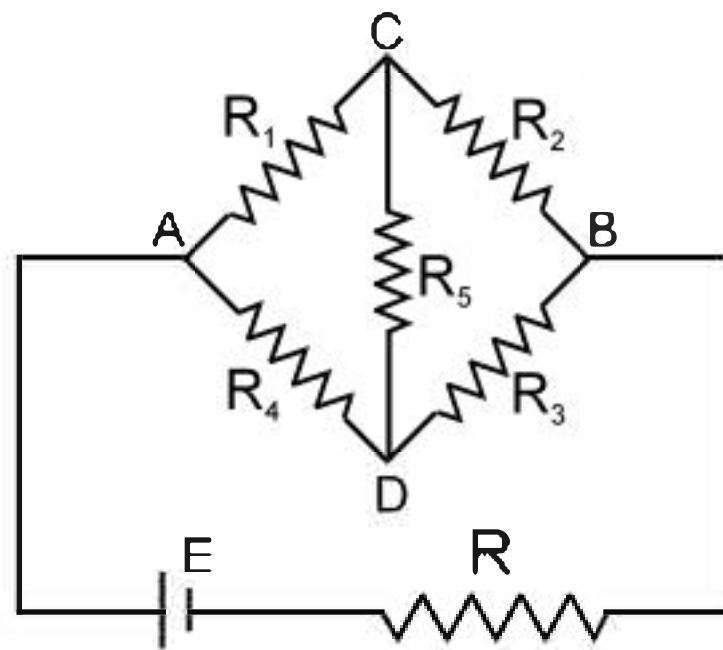
## 11. WHEATSTONE NETWORK : (4 TERMINAL NETWORK)




When current through the galvanometer is zero (null point or balance

point)  $\frac{P}{Q} = \frac{R}{S}$ , then  $PS = QR$

## 13. GROUPING OF CELLS

### 13.1 Cells in Series :

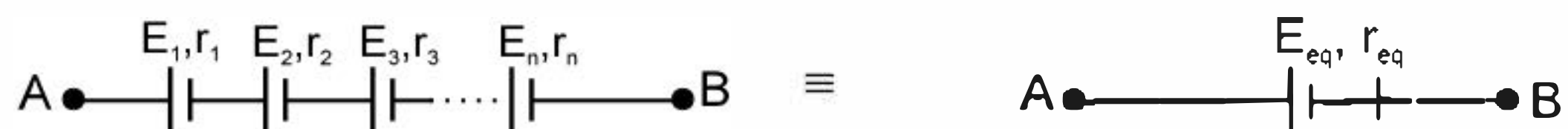


Equivalent EMF  $E_{eq} = E_1 + E_2 + \dots + E_n$  [write EMF's with polarity]

Equivalent internal resistance  $r_{eq} = r_1 + r_2 + r_3 + r_4 + \dots + r_n$
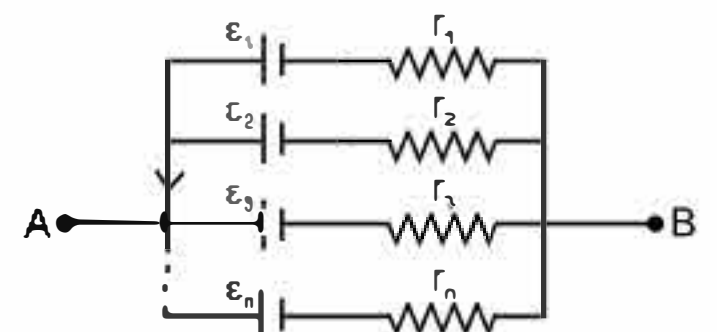
### 13.2 Cells in Parallel:


$$E_{eq} = \frac{\frac{\epsilon_1}{r_1} + \frac{\epsilon_2}{r_2} + \dots + \frac{\epsilon_n}{r_n}}{\frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}} \quad [\text{Use emf with polarity}]$$




$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$
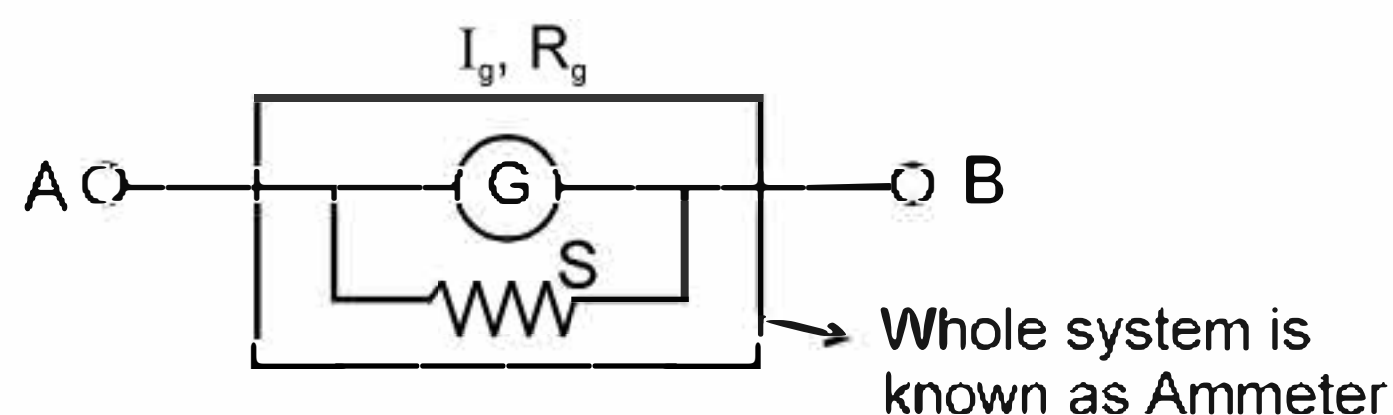
## 15. AMMETER

A shunt (small resistance) is connected in parallel with galvanometer to convert it into ammeter. An ideal ammeter has zero resistance



Ammeter is represented as follows -

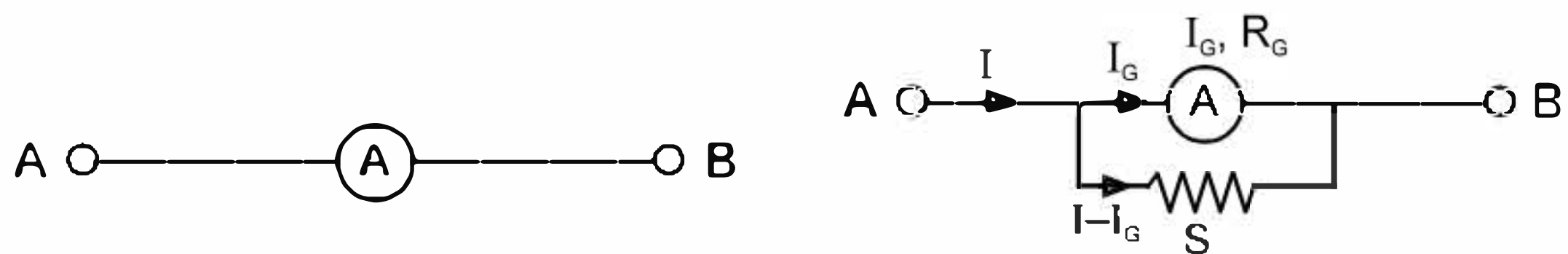

If maximum value of current to be measured by ammeter is  $I$  then


$$I_G \cdot R_G = (I - I_G)S$$

$$S = \frac{I_G \cdot R_G}{I - I_G} \quad S = \frac{I_G \times R_G}{I} \quad \text{when } I \gg I_G$$

where  $I$  = Maximum current that can be measured using the given ammeter.
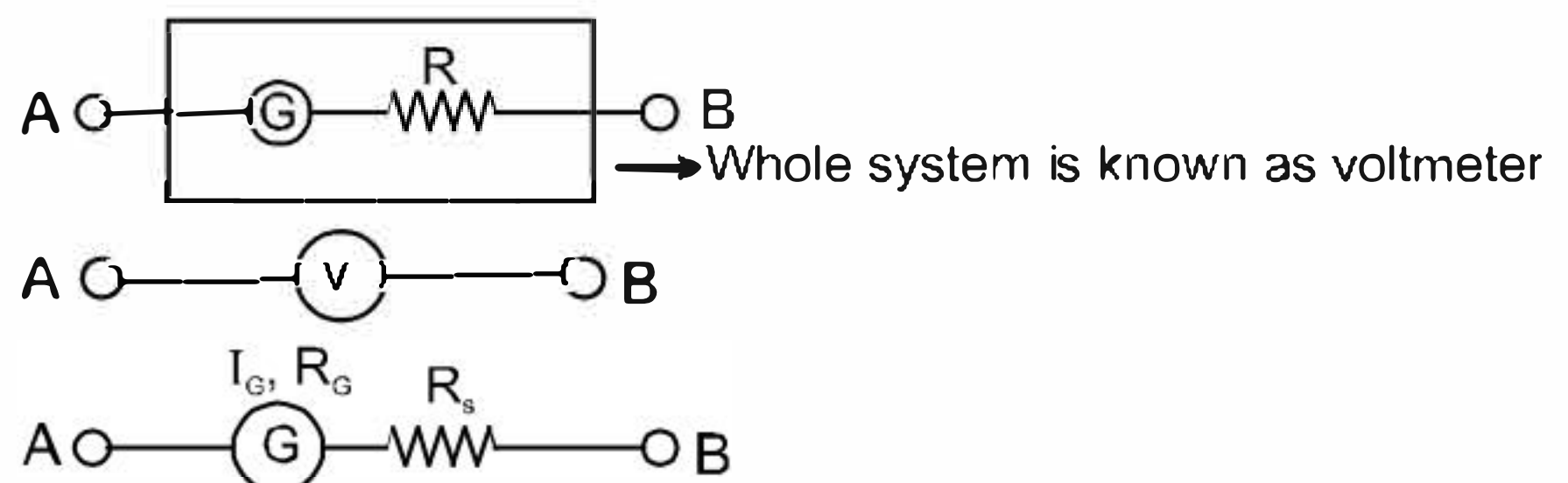
## 16. VOLTMETER

A high resistance is put in series with galvanometer. It is used to measure potential difference across a resistor in a circuit.




For maximum potential difference

$$V = I_G \cdot R_s + I_G R_G$$

$$R_s = \frac{V}{I_G} - R_G \quad \text{If } R_G \ll R_s \Rightarrow R_s \approx \frac{V}{I_G}$$

## 17. POTENTIOMETER

$$I = \frac{\varepsilon}{r + R}$$

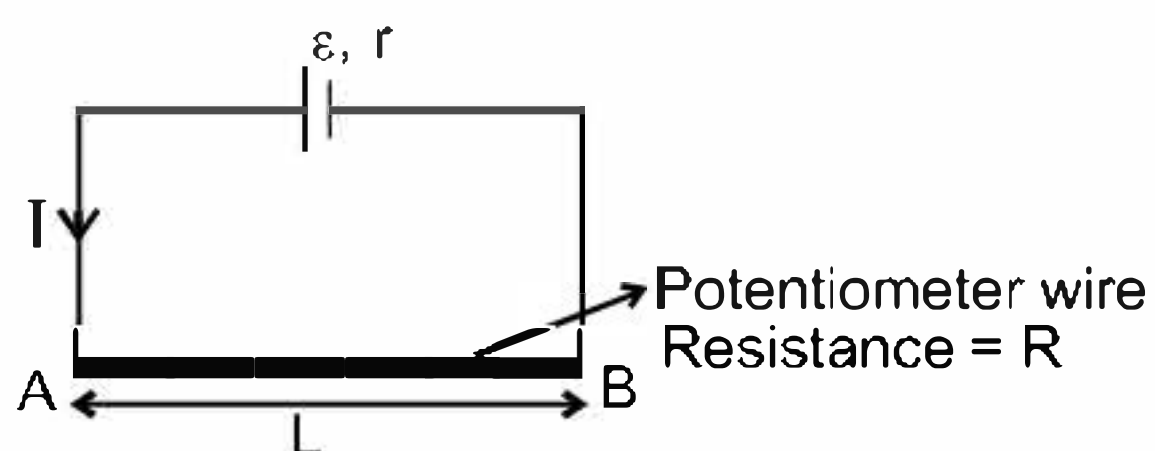

$$V_A - V_B = \frac{\varepsilon}{R + r} \cdot R$$

Potential gradient ( $x$ ) → Potential difference per unit length of wire

$$x = \frac{V_A - V_B}{L} = \frac{\varepsilon}{R + r} \cdot \frac{R}{L}$$

## Application of potentiometer

(a) To find emf of unknown cell and compare emf of two cells.


In case I,

In figure (1) is joint to (2) then balance length =  $\ell_1$   
 $\varepsilon_1 = x\ell_1$  ....(1)

in case II,

In figure (3) is joint to (2) then balance length =  $\ell_2$   
 $\varepsilon_2 = x\ell_2$  ....(2)
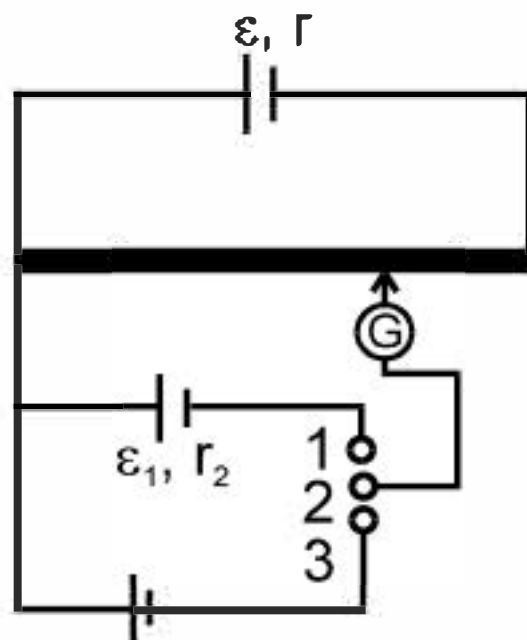
$$\frac{\varepsilon_1}{\varepsilon_2} = \frac{\ell_1}{\ell_2}$$




If any one of  $\varepsilon_1$  or  $\varepsilon_2$  is known the other can be found. If  $x$  is known then both  $\varepsilon_1$  and  $\varepsilon_2$  can be found

(b) To find current if resistance is known

$$V_A - V_C = x\ell_1$$

$$IR_1 = x\ell_1$$

$$I = \frac{x\ell_1}{R_1}$$

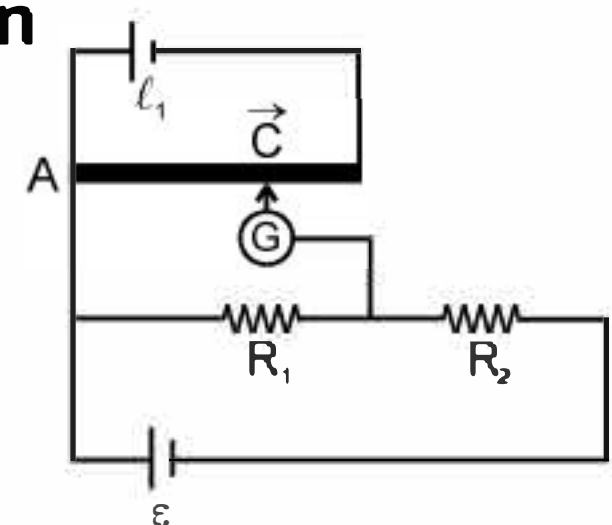



Similarly, we can find the value of  $R_2$  also.

Potentiometer is ideal voltmeter because it does not draw any current from circuit, at the balance point.

(c) To find the internal resistance of cell.

1<sup>st</sup> arrangement

2<sup>nd</sup> arrangement

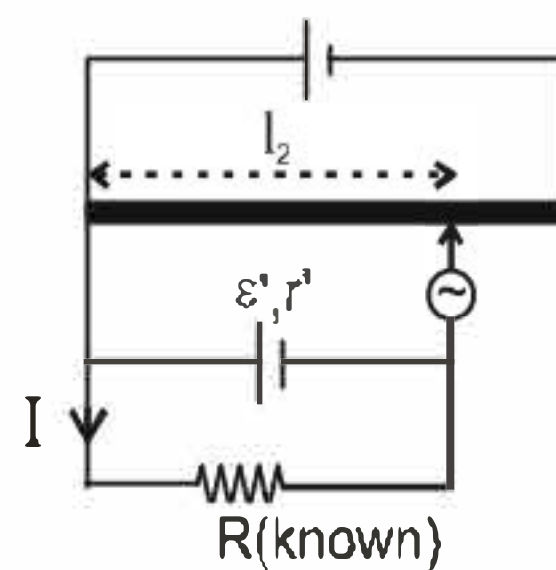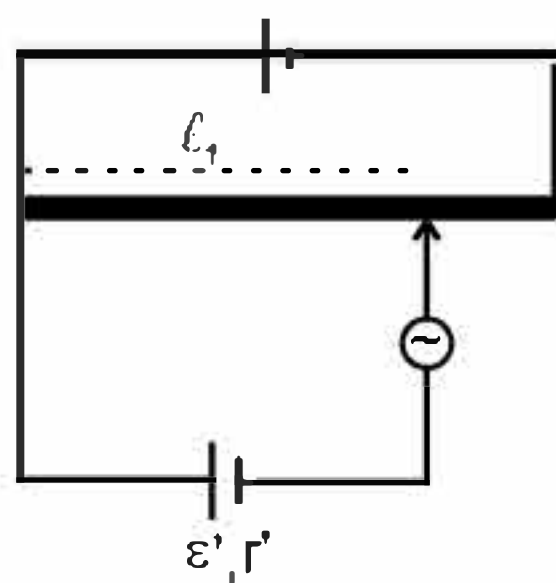



by first arrangement  $\varepsilon' = x\ell_1$  ... (1)  
 by second arrangement  $IR = x\ell_2$

$$I = \frac{x\ell_2}{R}, \quad \text{also } I = \frac{\varepsilon'}{r' + R}$$

$$\therefore \frac{\varepsilon'}{r' + R} = \frac{x\ell_2}{R} \Rightarrow \frac{x\ell_1}{r' + R} = \frac{x\ell_2}{R}$$

$$r' = \left[ \frac{\ell_1 - \ell_2}{\ell_2} \right] R$$

(d) Ammeter and voltmeter can be graduated by potentiometer.

(e) Ammeter and voltmeter can be calibrated by potentiometer.

### 18. METRE BRIDGE (USE TO MEASURE UNKNOWN RESISTANCE)



If  $AB = \ell$  cm, then  $BC = (100 - \ell)$  cm.

Resistance of the wire between A and B,  $R \propto \ell$

[  $\because$  Specific resistance  $\rho$  and cross-sectional area  $A$  are same for whole of the wire ]

$$\text{or } R = \sigma \ell \quad \dots (1)$$

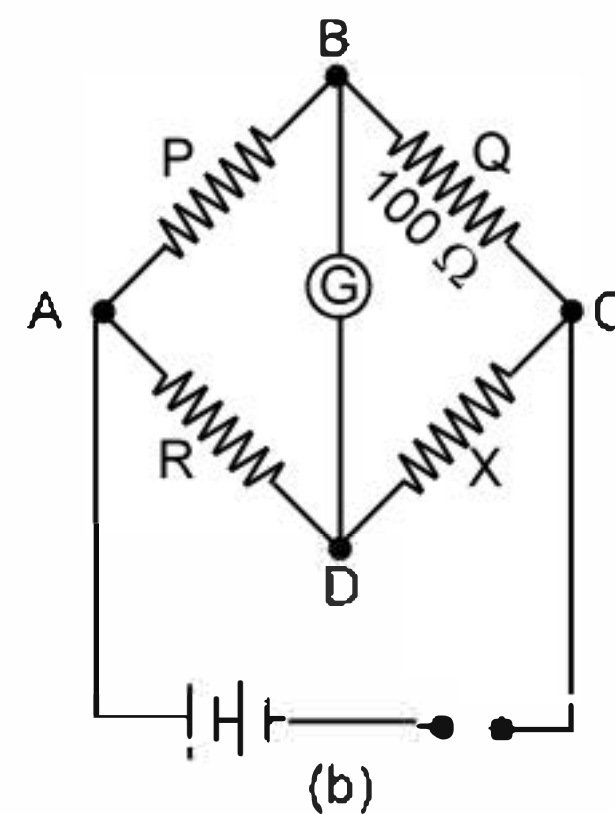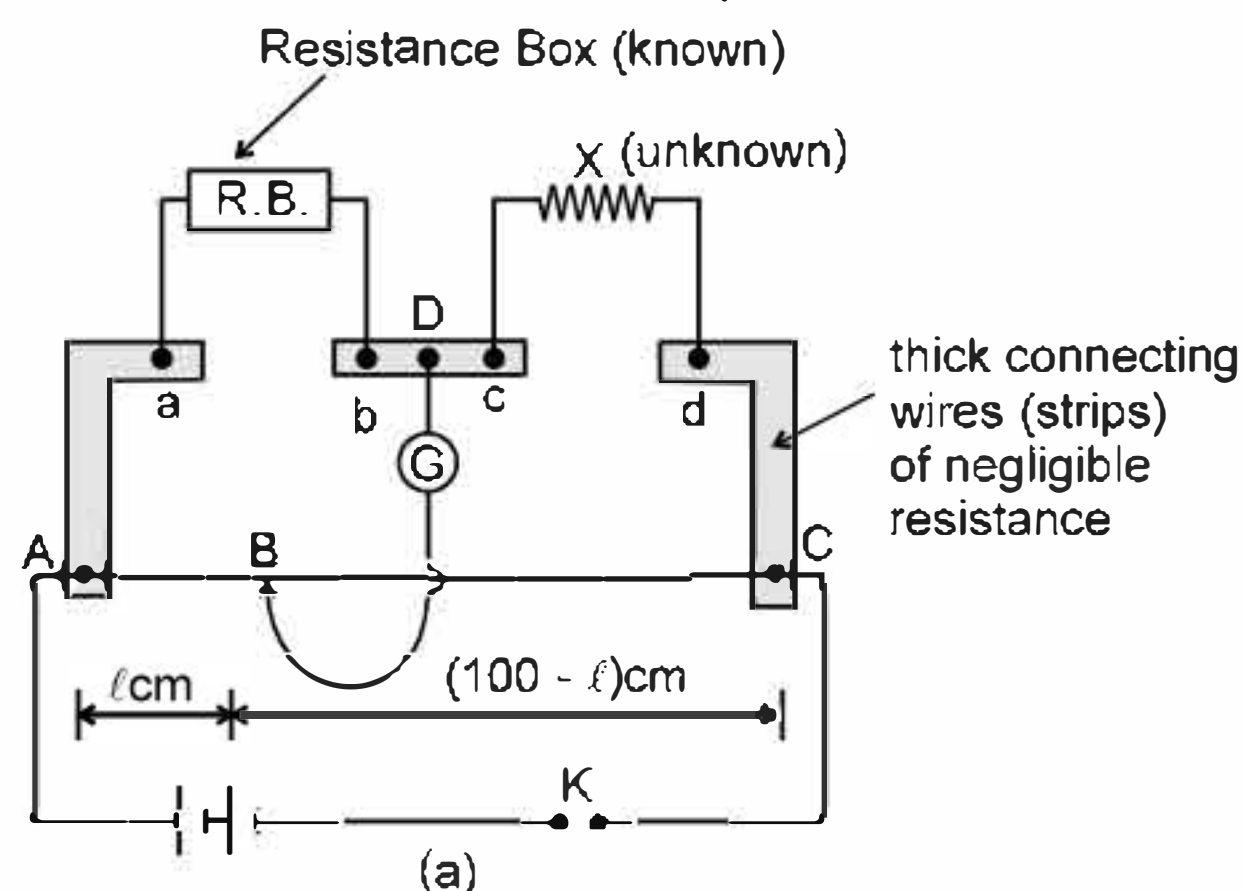where  $\sigma$  is resistance per cm of wire.



If  $P$  is the resistance of wire between A and B then

$$P \propto \ell \Rightarrow P = \sigma(\ell)$$

Similarly, if  $Q$  is resistance of the wire between B and C, then

$$Q \propto 100 - \ell$$

$$\therefore Q = \sigma(100 - \ell) \quad \dots (2)$$

Dividing (1) by (2),

$$\frac{P}{Q} = \frac{\ell}{100 - \ell}$$

Applying the condition for balanced Wheatstone bridge, we get  $RQ = PX$

$$\therefore x = R \frac{Q}{P} \quad \text{or} \quad X = \frac{100 - \ell}{\ell} R$$

Since  $R$  and  $\ell$  are known, therefore, the value of  $X$  can be calculated.